



Faculty of Engineering & Technology
Department of Electrical & Computer Engineering
ENEE2103-Circuit And Electronics Laboratory
PreLab#2

Prepared by:

Saja Asfour 1210737

Instructor:

Mr.Nasser Ismail

Assistance:

Eng. Hazem Awaysa

Section:

Sec1

Date:

27/2/2024

Contents

Figure:	2
A- KVL,KCL:	3
B-Voltage & current Division:.....	4
I. Voltage division:	4
II. Current division:	5
c. superposition:	7
D-Thevinin and Norton equivalent circuits:	8

Figure:

Figure1 :Kvl,Kcl with $R_x=1k$	3
Figure 2:Kvl,Kcl with $R_x=0.5k$	3
Figure3 :voltage division circuit with $R_x=1k$	4
Figure4 : voltage division circuit with $R_x=0.5k$	5
Figure 5: current division with $R_x=1k$	5
Figure 6: current division when $R_x=0.5k$	6
Figure7 :superposition circuit with $v_{s1}=5$ & $v_{s2}=10$	7
Figure 8:superposition when kill V_{s1}	7
Figure 9:superposition when kill v_{s2}	8
Figure 10:circuit to find V_{R1}	8
Figure 11:circuit to find V_{oc}	9
Figure 12:circuit to find I_{sc}	9
Figure 13:circuit to find R_{th}	9
Figure 14:thevinin equivalent circuit	10
Figure 15: circuit to find I_{ab} from thevinin	10
Figure 16:connect R_1 to thevinin equivalent circuit.....	11
Figure17 : Nortan equivalent circuit	11

A- KVL,KCL:

Consider $R_x=R1=R4=1k\Omega$, $R5=3.3k\Omega$, $R6=4.7k\Omega$

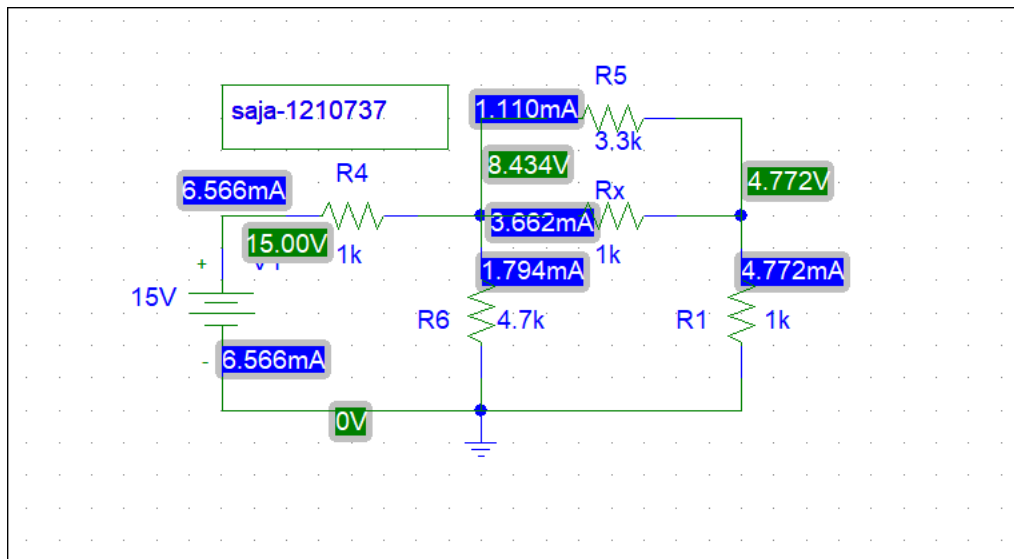


Figure1 :Kvl,Kcl with $R_x=1k$

For voltage:

$V1=4.772\text{volt}$

$V6=8.434\text{volt}$

By KVL:

$V4=15-8.434=6.566\text{volt}$

$V5=V_x=8.434-4.772=3.662\text{volt (in parallel)}$.

Test For current:

$I4=6.566\text{mA}$

By KCL:

$I4=I5+I_x+I6$

$1.110+3.662+1.794=6.566\text{mA}$

$I5+I_x=I1$

$1.110+3.662=4.772\text{mA}$

Change the value of R_x to the half of the first value.

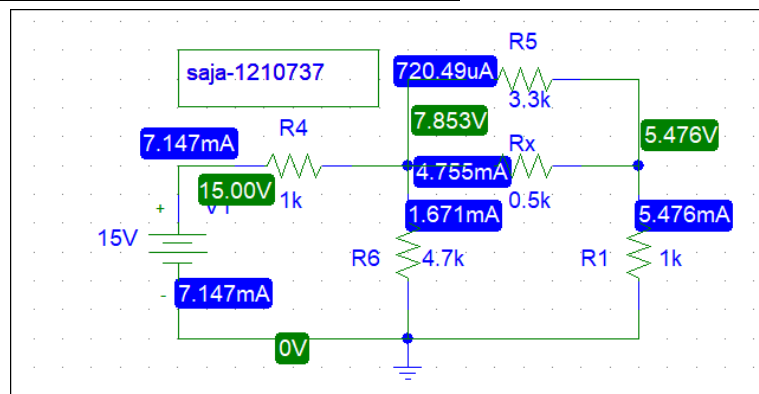


Figure 2:Kvl,Kcl with $R_x=0.5k$

For voltage:

$V_1 = 5.476\text{volt}$

$V_6 = 7.853\text{volt}$

By KVL:

$V_4 = 15 - 7.853 = 7.147\text{volt}$

$V_5 = V_x = 7.853 - 5.476 = 2.377\text{volt}$

Test For current:

$I_4 = 7.147\text{mA}$

By KCL:

$I_4 = I_5 + I_x + I_6$

$0.72049 + 4.755 + 1.671 = 7.14649\text{mA}$

$I_5 + I_x = I_1$

$0.72049 + 4.755 = 5.47549\text{mA}$

In two case the simulation result match the expected result.

B-Voltage & current Division:

I. Voltage division:

Consider $R_x = R_1 = R_4 = 1\text{k}\Omega$, $R_6 = 4.7\text{k}\Omega$

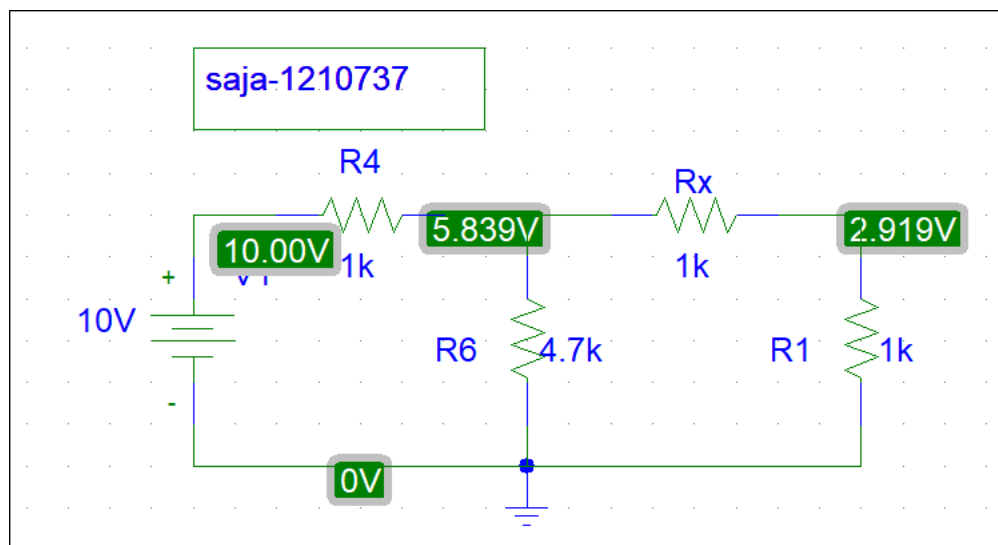


Figure3 :voltage division circuit with $R_x = 1\text{k}$

$V_s = 10\text{volt}$

$R_x + R_1 = 2\text{k}$

$2\text{k} // R_6 = 1.402\text{k}$

$V_6 = V_s * 1.402 / (1.402 + 1) = 5.836\text{volt}$ by voltage divider rule.

$V_4 = V_s * 1 / (1.402 + 1) = 4.163\text{volt}$

$V_x = V_6 * R_x / (R_1 + R_x) = 2.918\text{volt}$

$V_1 = V_6 * R_1 / (R_1 + R_x) = 2.918\text{volt}$

Consider $R_x=0.5k$, $R_1=R_4=1k\Omega$, $R_6=4.7k\Omega$

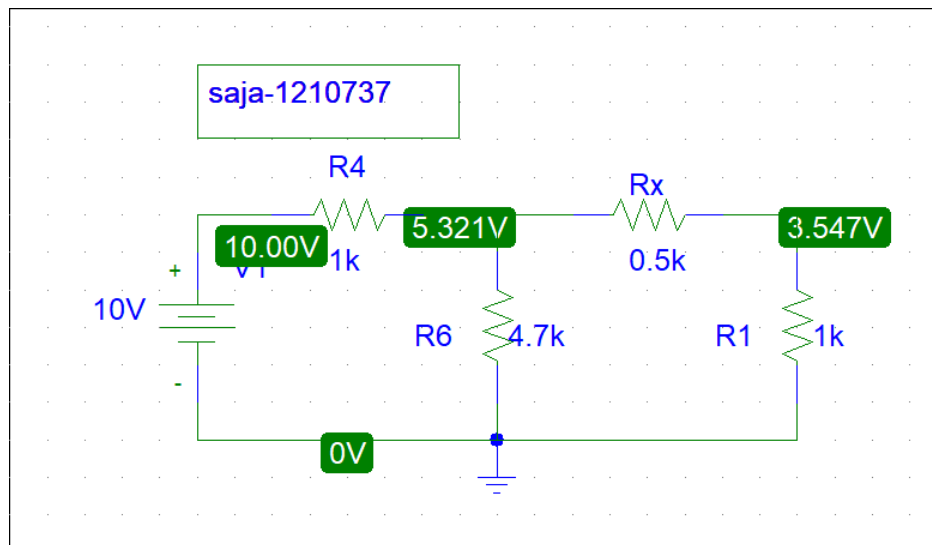


Figure4 : voltage division circuit with $R_x=0.5k$

$V_s=10\text{volt}$

$R_x+R_1=1.5k$

$1.5k//R_6=1.137k$

$V_6=V_s*1.137/(1.137+1)=5.321\text{volt}$ by voltage divider rule.

$V_4=V_s*1/(1.137+1)=4.679\text{volt}$

$V_x=V_6*R_x/(R_1+R_x)=1.774\text{volt}$

$V_1=V_6*R_1/(R_1+R_x)=3.547\text{volt}$

The result in simulation is match the expected result .

II. Current division:

When $R_x=1k$:

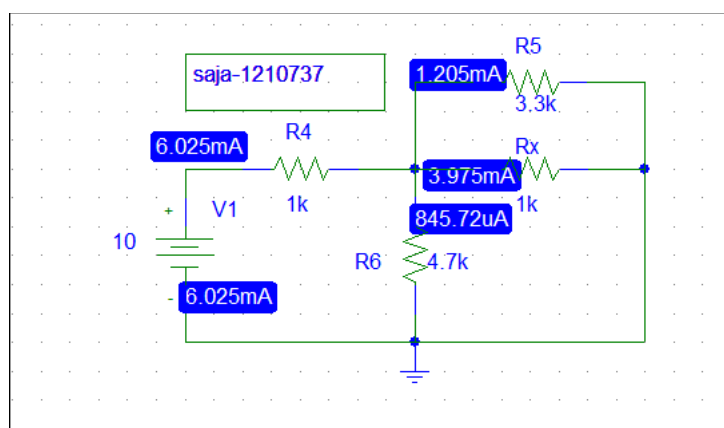


Figure 5: current division with $R_x=1k$

$R_{eq}=R_4+[R_5//R_6//R_x]=1.66k$

$I_4=V_s/R_{eq}=6.024\text{mA}$

$$R_x/R_6=0.824k$$

$$I_5=I_4*0.824/(0.824+3.3)=1.204mA$$

$$R_x/R_5=0.767k$$

$$I_6=I_4*0.767/(0.767+4.7)=0.845mA$$

$$R_5/R_6=1.939k$$

$$I_x=I_4*1.939/(1.939+1)=3.974mA$$

When $R_x=0.5k$

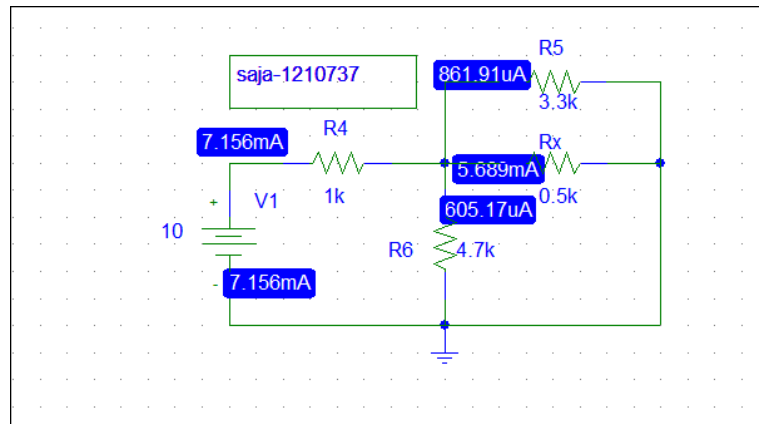


Figure 6: current division when $R_x=0.5k$

$$R_{eq}=R_4+[R_5/R_6/R_x]=1.397k$$

$$I_4=V_s/R_{eq}=7.158mA$$

$$R_x/R_6=0.452k$$

$$I_5=I_4*0.452/(0.452+3.3)=0.862mA$$

$$R_x/R_5=0.434k$$

$$I_6=I_4*0.434/(0.434+4.7)=0.605mA$$

$$R_5/R_6=1.939k$$

$$I_x=I_4*1.939/(1.939+0.5)=5.690mA$$

The result in simulation is match the expected result .

c. superposition:

when $V_{s1}=5\text{volt}$ and $v_{s2}=10\text{volt}$

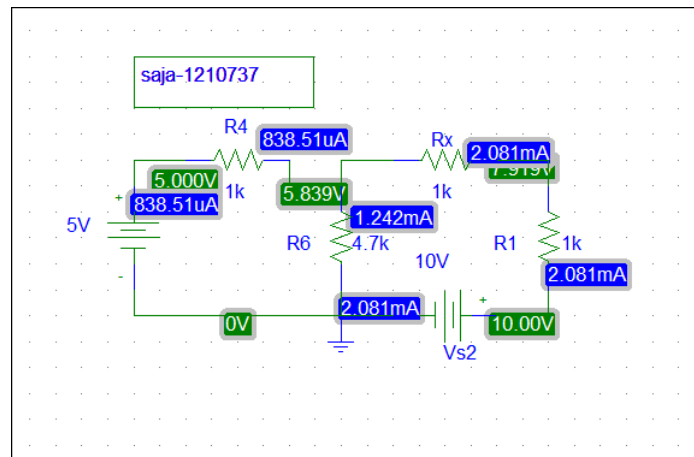


Figure7 :superposition circuit with $v_{s1}=5$ & $v_{s2}=10$

When $V_{s1}=0$ and $V_{s2}=10$

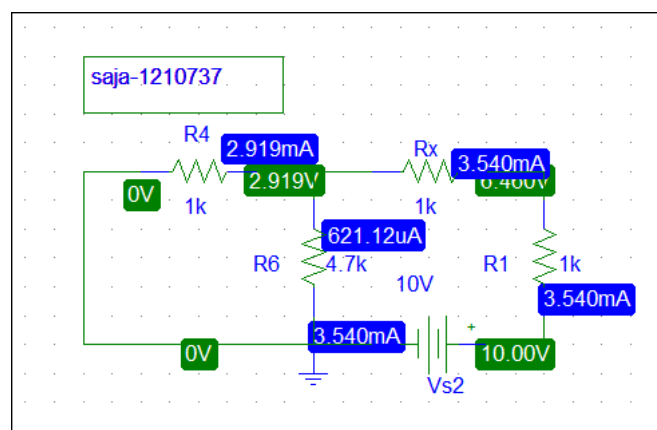


Figure 8:superposition when kill V_{s1}

$$R4//R6=0.825k$$

$$V6'=V_{s2} \cdot 0.825 / (0.825 + R_x + R1) = 2.92\text{volt}$$

$$I6'=V6'/R6=0.621\text{mA}$$

When $V_{s1}=5$ & $V_{s2}=0$:

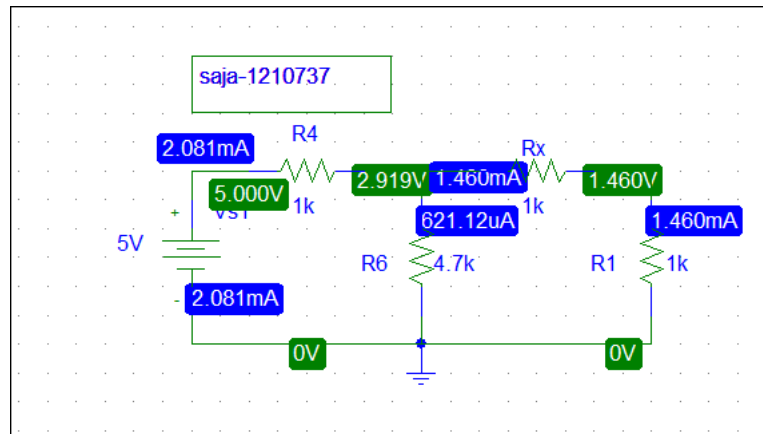


Figure 9:superposition when kill v_{s2}

$$[R_x + R_1] // R_6 = 1.403k$$

$$V_6'' = V_{s1} * 1.403 / (1.403 + R_4) = 2.919 \text{ volt}$$

$$I_6'' = V_6'' / R_6 = 0.621 \text{ mA}$$

$$V_6 = V_6' + V_6'' = 2.92 + 2.919 = 5.839 \text{ volt}$$

$$I_6 = I_6' + I_6'' = 0.621 + 0.621 = 1.242 \text{ mA}$$

The result in simulation is match the expected result .

D-Thevinin and Norton equivalent circuits:

1. Set the V_{s1} to 5volts and V_{s2} to 10 volts and measure voltage across R_1 .

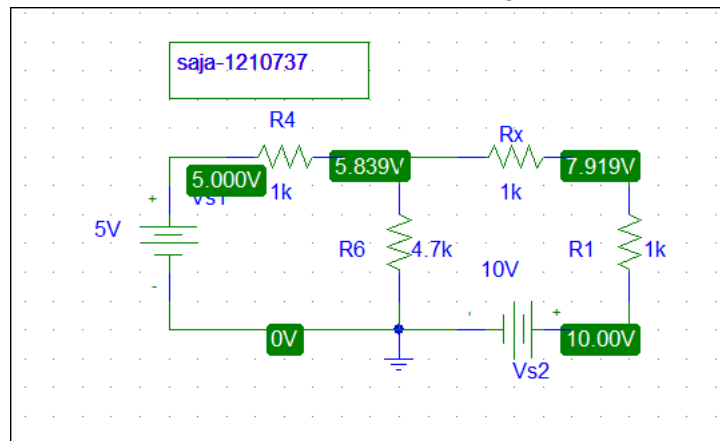


Figure 10:circuit to find V_{R1}

$$V_{R1} = V_{s2} - V_{R_x} = 10 - 7.919 = 2.081 \text{ volt}$$

2. Disconnect R1 and measure the voltage on the terminals (a,b) .[Voc- open circuit voltage]

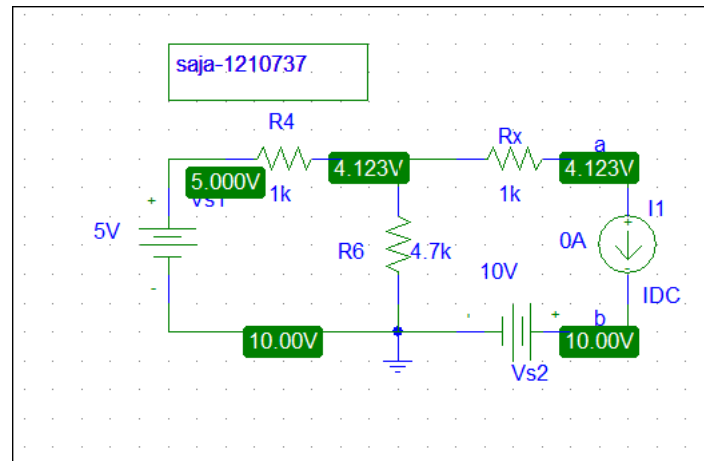


Figure 11:circuit to find Voc

$$V_{oc} = 10 - 4.123 = 5.877 \text{ volt}$$

3. Short circuit the terminals (a, b) and measure the current in the short circuit (Isc)

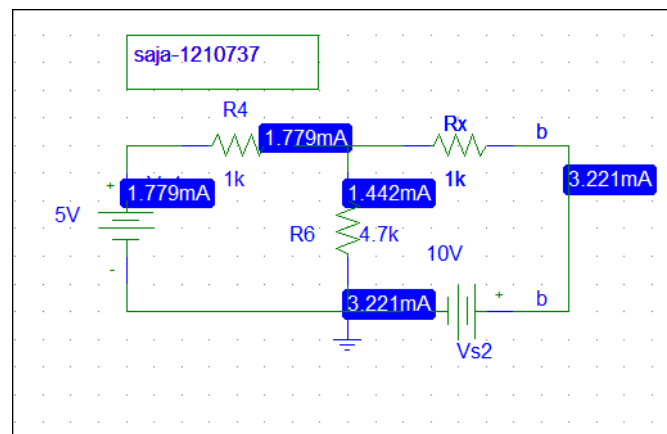


Figure 12:circuit to find Isc

$$I_{sc} = I_x = 3.221 \text{ mA}$$

4. Disconnect the voltage sources and short circuit the terminals where each source was connected and Measure the resistance from the terminals (a,b) ($R_{ab} = R_{th}$).

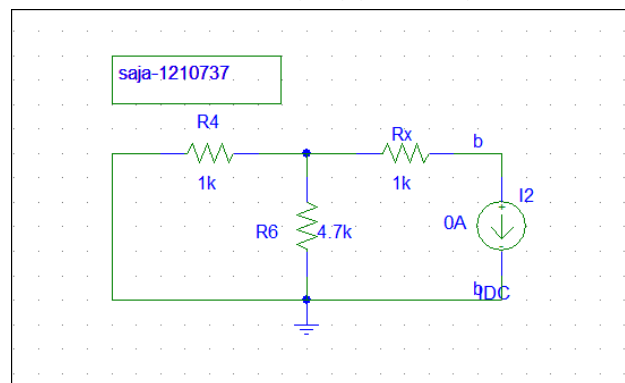


Figure 13:circuit to find Rth

$$R_{th} = [R_x // R_6] + R_4 = 1.825k$$

5. connect the thevinin equivalent circuit:

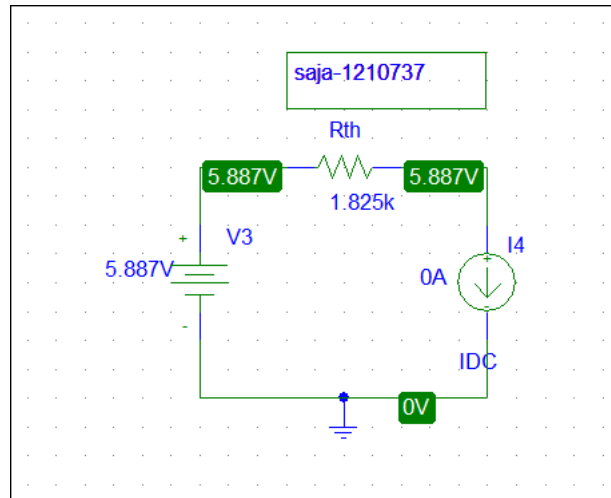


Figure 14: thevinin equivalent circuit

$$V_{ab} = V_{oc} + V_{Rth} = 5.887 + 0 = 5.887 \text{ volt}$$

6- . Short circuit the terminals of the series connection and measure the current in the short circuit

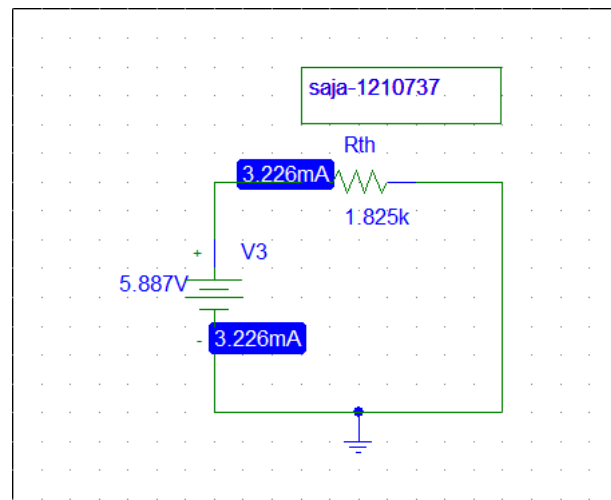


Figure 15: circuit to find Iab from thevinin

$$I_{ab} = V_{oc} / R_{th} = 3.226 \text{ mA}$$

the relation between the voltage values measured in steps (2,5) → they are equal.

the relation between the voltage values measured in steps (3,6) → they are equal.

7. Connect the resistance R1 across terminal a-b and measure the voltage across it

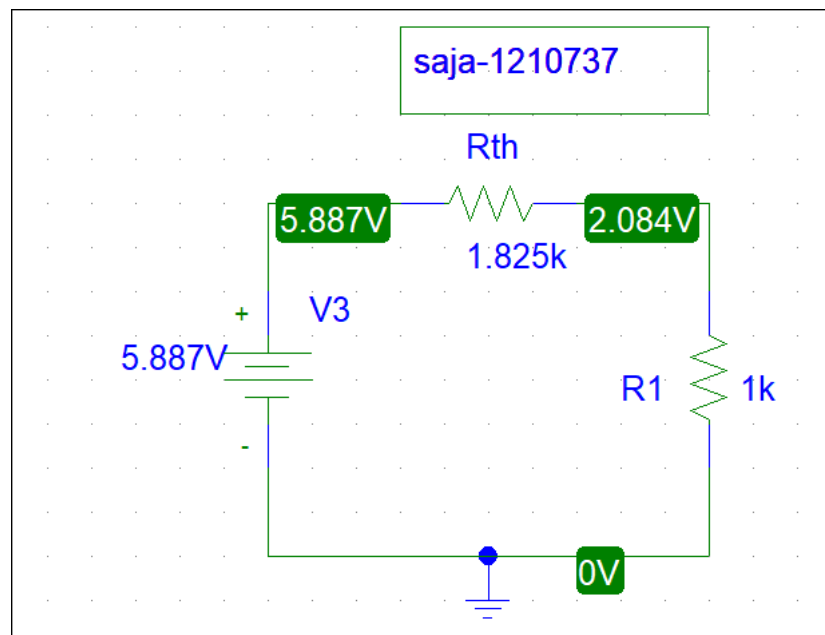


Figure 16: connect R1 to thevenin equivalent circuit

$$V_{R1} = V_{oc} \cdot R_1 / [R_1 + R_{th}] = 2.084V$$

The value in this step is equal to the value in step 1

The result in simulation matches the expected result.

8. Compare the short circuit current value with the Norton current source determined by computation

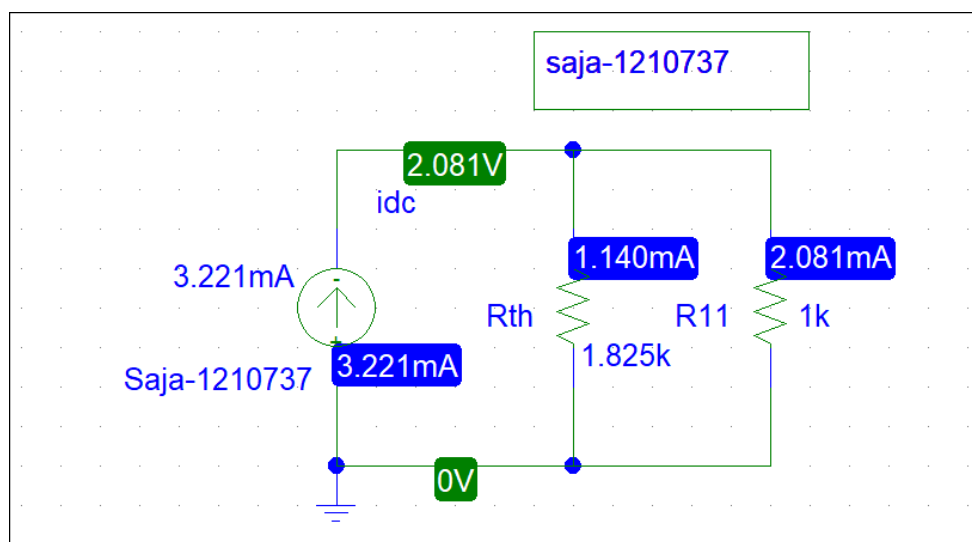


Figure 17 : Norton equivalent circuit