



Faculty of Engineering & Technology
Department of Electrical & Computer Engineering
ENEE2103-Circuit And Electronics Laboratory
PreLab#7

Prepared by:

Saja Asfour 1210737

Instructor:

Mr.Nasser Ismail

Assistance:

Eng. Hazem Awaysa

Section:

Sec1

Date:

29/3/2024

Table of Contents

Table of Figures:	2
List of Tables:	3
Part one: CE amplifier with voltage divider - bias	4
Part two: COMMON COLLECTER TRANSISTOR AMPLIFIER.....	10

Table of Figures:

Figure1 : Part1 Circuit in PsPice.....	4
Figure 2:part1 potentiometer settings	4
Figure 3:part1 Vsin settings	5
Figure 4:Part1 circuit Voltage.....	5
Figure 5:Part1 circuit current	6
Figure 6:part1 new Vsin setting	6
Figure 7:part1 Vi and Vo Waveform	7
Figure 8:part1 Vsin setting to have Vout=4v.....	7
Figure 9:part1 Vi and Vo Waveform to have Vo=4V	7
Figure 10:Part1 circuit to find Av1	8
Figure 11:part1 Vo and VB waveform to find Av1	8
Figure 12:Part1 circuit without 100k resistor	8
Figure 13:part1 Vi and Vo waveform without 100k.....	9
Figure 14:CC circuit	10
Figure 15:CC circuit Vsin setting	10
Figure 16:CC circuit voltage.....	11
Figure 17:CC circuit Current	11
Figure 18:CC Vo and Vi waveforms in order to calculate the gain.....	12
Figure 19:CC Vi and Vo waveforms when Vo = 2V peak-to-peak.....	12
Figure 20:CC Input and output currents	12
Figure 21:CC Output impedance measuring circuit	13
Figure 22:CC output voltage and current for the impedance.....	13

List of Tables:

Table 1: CC measured and calculated value	14
---	----

Part one: CE amplifier with voltage divider - bias

The PCPICE circuit is displayed in the figure below, with the amplitude of the AC voltage source amplitude equals 0v, and frequency 1kHz.

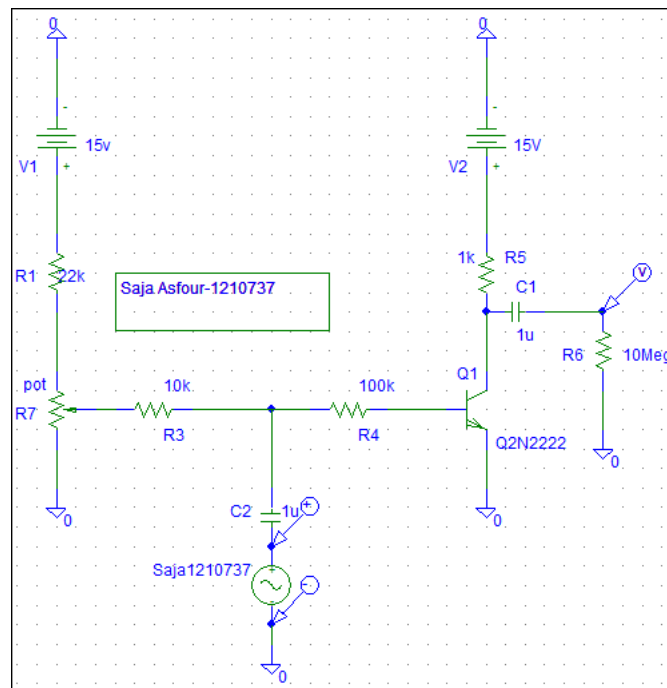


Figure1 : Part1 Circuit in PsPice

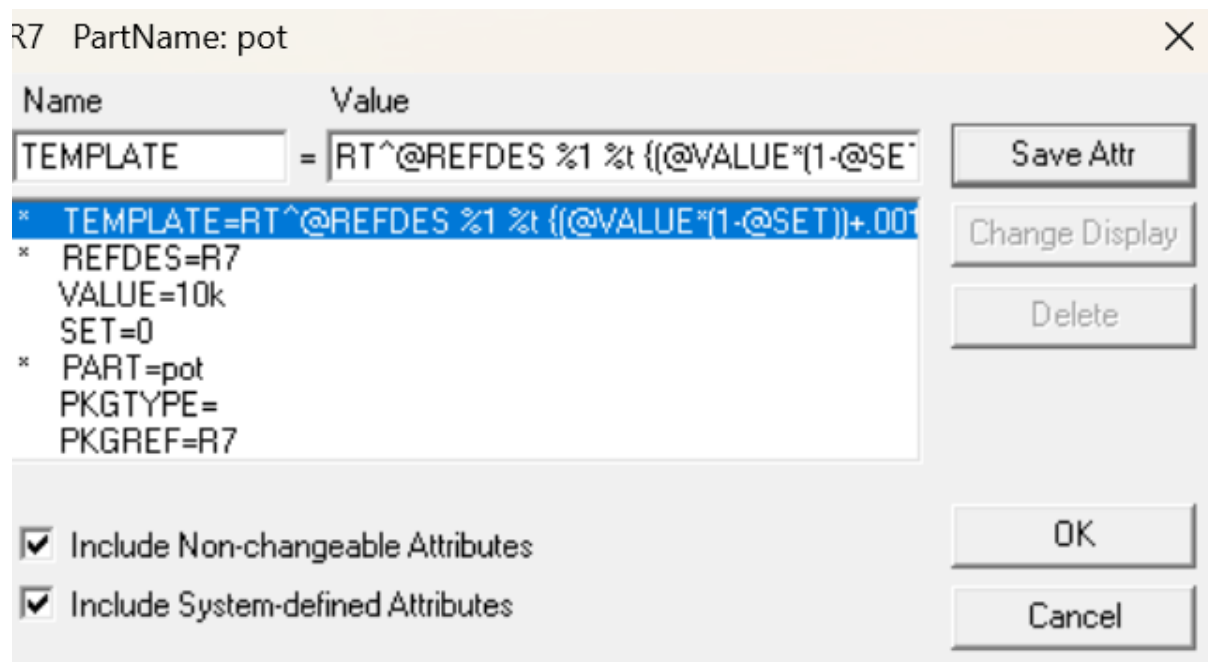


Figure 2:part1 potentiometer settings

V4 PartName: vsin

Name	Value
REFDES	= V4

* TEMPLATE=V^@REFDES %+ %- ?DC|DC @DC| ?AC|AC @
 DC=0
 AC=0
 VOFF=0
 VAMPL=0
 FREQ=1k
 TD=0

☒ Include Non-changeable Attributes
☒ Include System-defined Attributes

Save Attr
 Change Display
 Delete
 OK
 Cancel

Figure 3:part1 Vsin settings

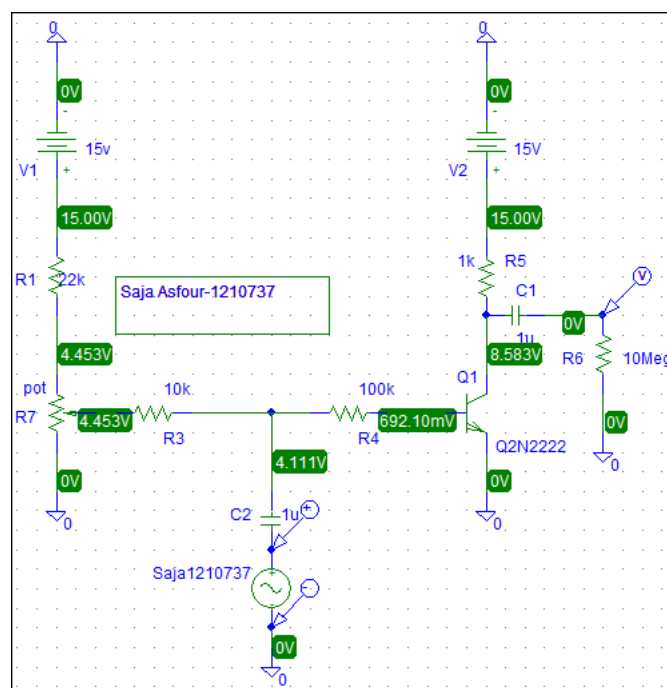


Figure 4:Part1 circuit Voltage

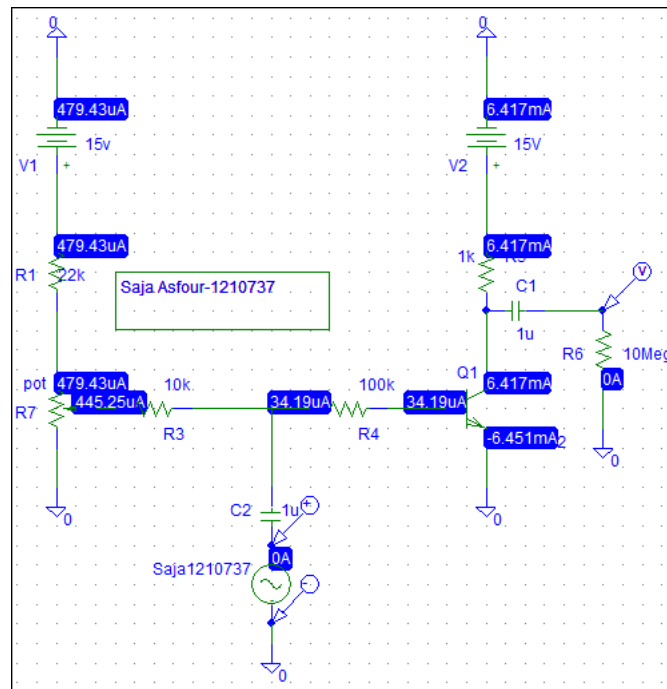


Figure 5:Part1 circuit current

As shown in the previous two figures:

$V_C = 8.583V$, $V_{BE} = V_B - V_E = 692.10 - 0 = 692.10mV$, $V_{CE} = V_C - V_E = 8.583 - 0 = 8.583V$,
 $I_C = 6.417mA$, $I_B = 34.19uA$.

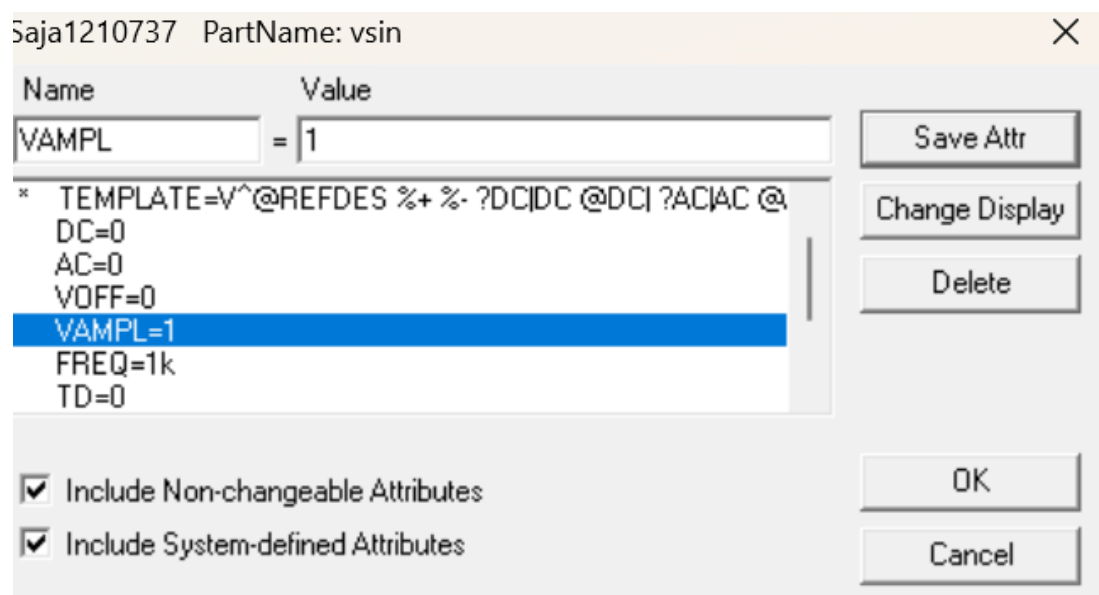


Figure 6:part1 new Vsin setting

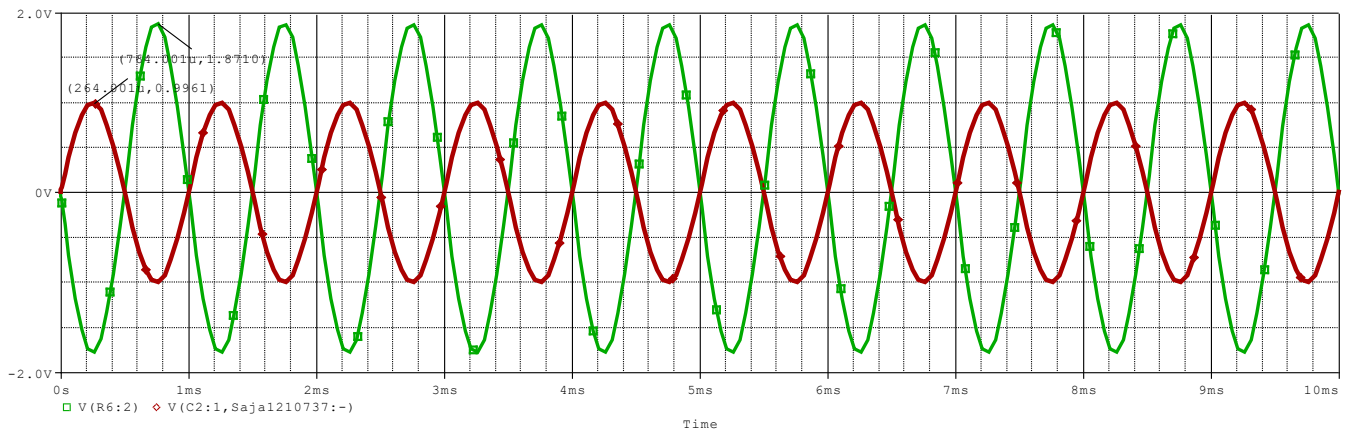


Figure 7:part1 Vi and Vo Waveform

The voltage gain equals $= V_o/V_{in} = 1.8710/0.9961 = 1.8783$, So, in order to have $V_o = 4v$ peak, V_{in} (to get $V_o = 4$) $= 4/1.8783 = 2.1295V$.

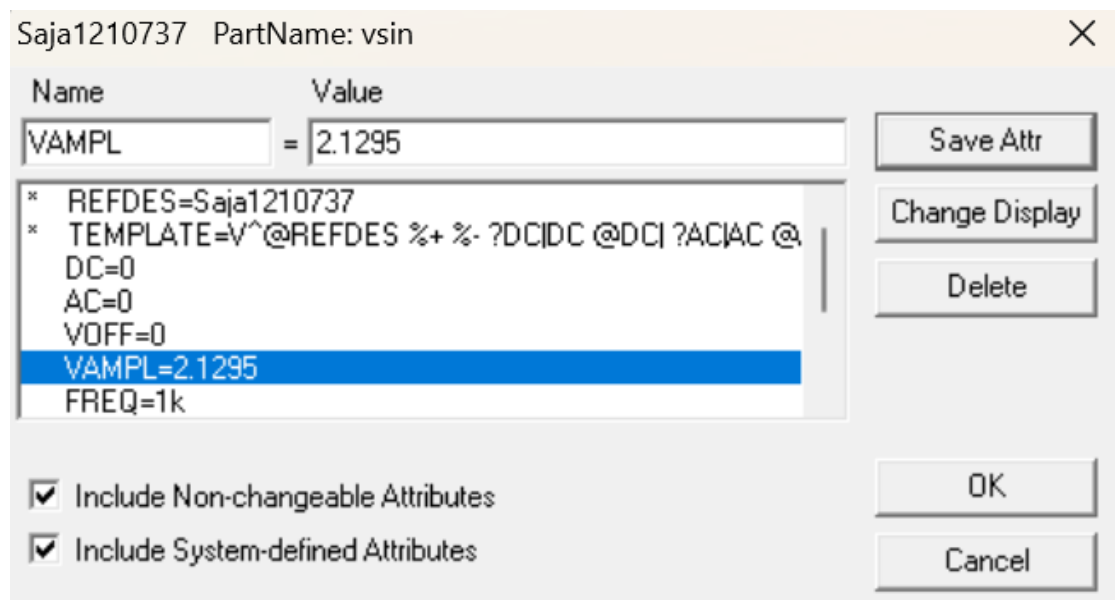


Figure 8:part1 Vsin setting to have $V_{out}=4v$

The plot of the input and output voltages when $V_{OUT} = 4$, is displayed in the figure below.

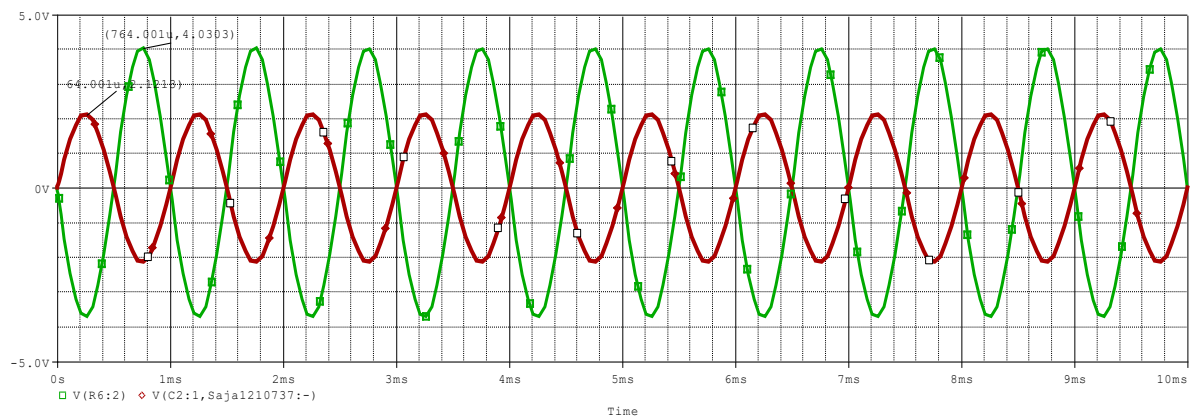


Figure 9:part1 Vi and Vo Waveform to have $V_o=4V$

Then to Calculate $A_{v1} = V_o(t)/V_B(t)$

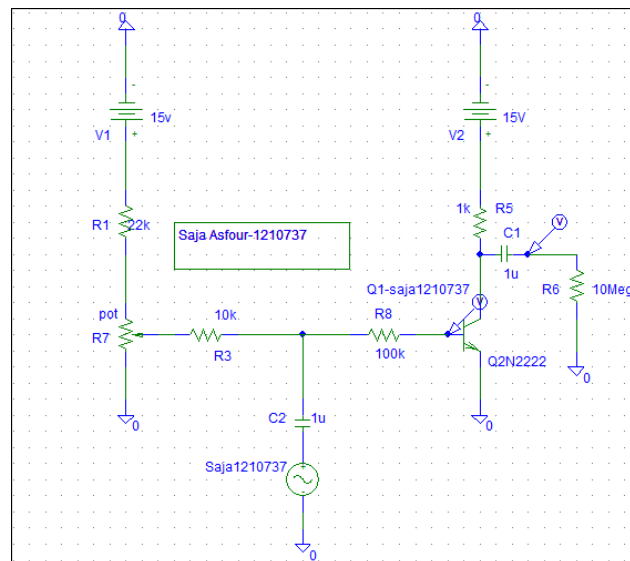


Figure 10:Part1 circuit to find A_{v1}

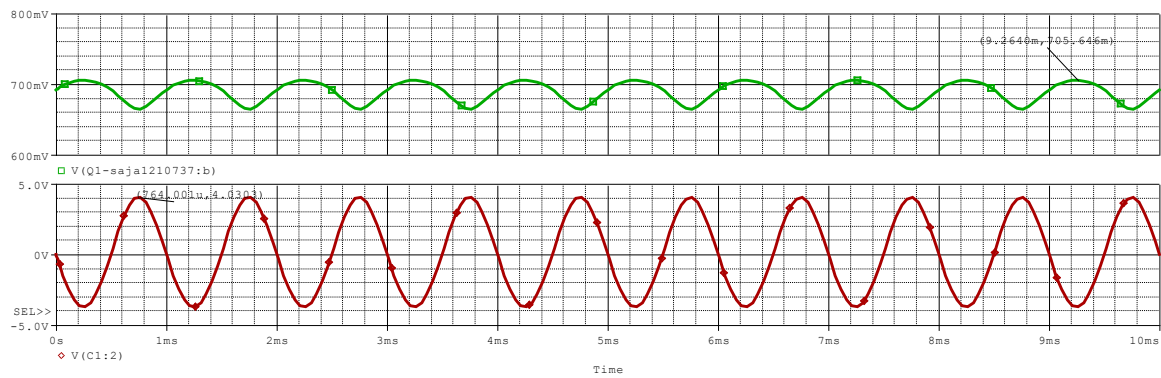


Figure 11:part1 V_o and V_B waveform to find A_{v1}

$$A_{v1} = V_o(t)/V_B(t) = 4.0303/705.646m = 5.7115$$

Then if I removed the resistor with value $100k\Omega$ like figure below:

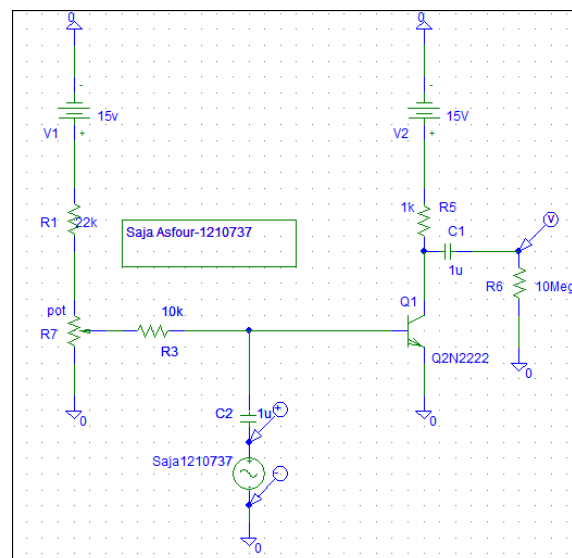


Figure 12:Part1 circuit without $100k$ resistor

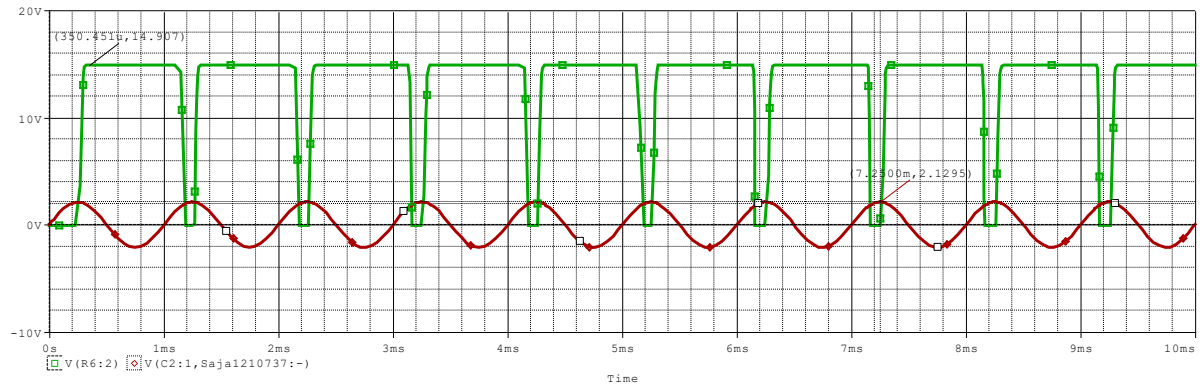


Figure 13:part1 Vi and Vo waveform without 100k

The voltage gain = $14.907/2.1295 = 7.0002$, which is much increased because vi is increased.

Part two: COMMON COLLECTOR TRANSISTOR AMPLIFIER

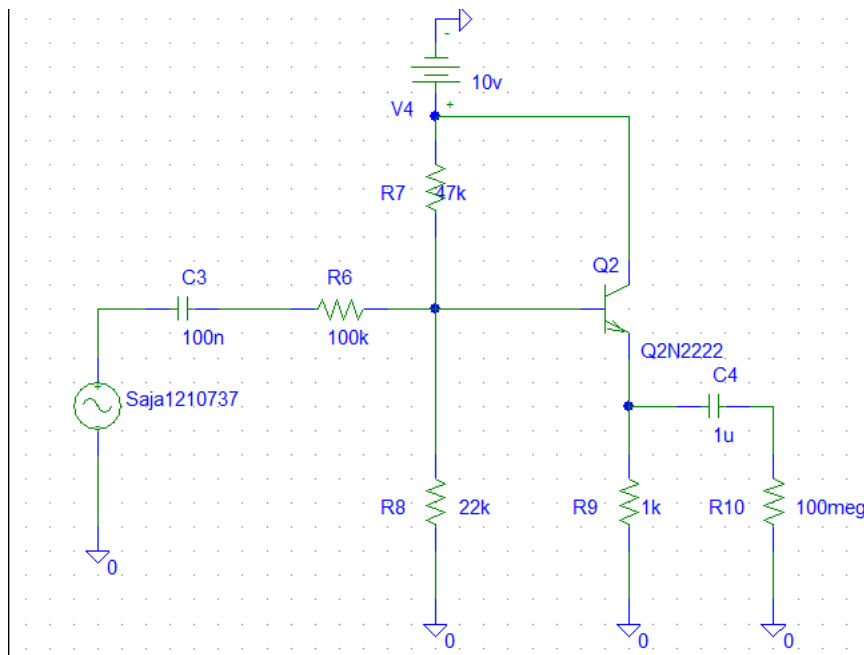


Figure 14:CC circuit

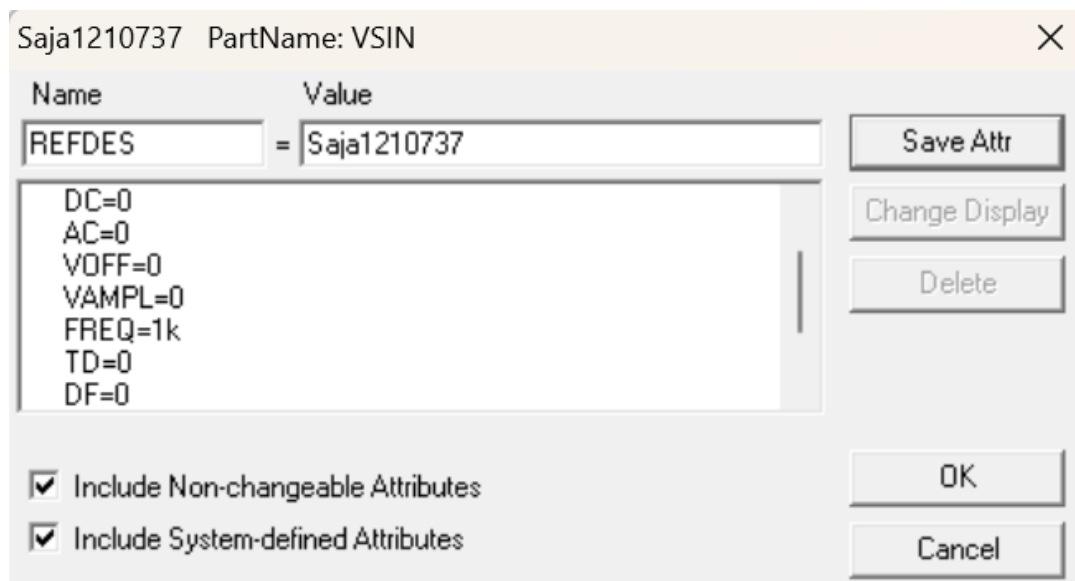


Figure 15:CC circuit Vsin setting

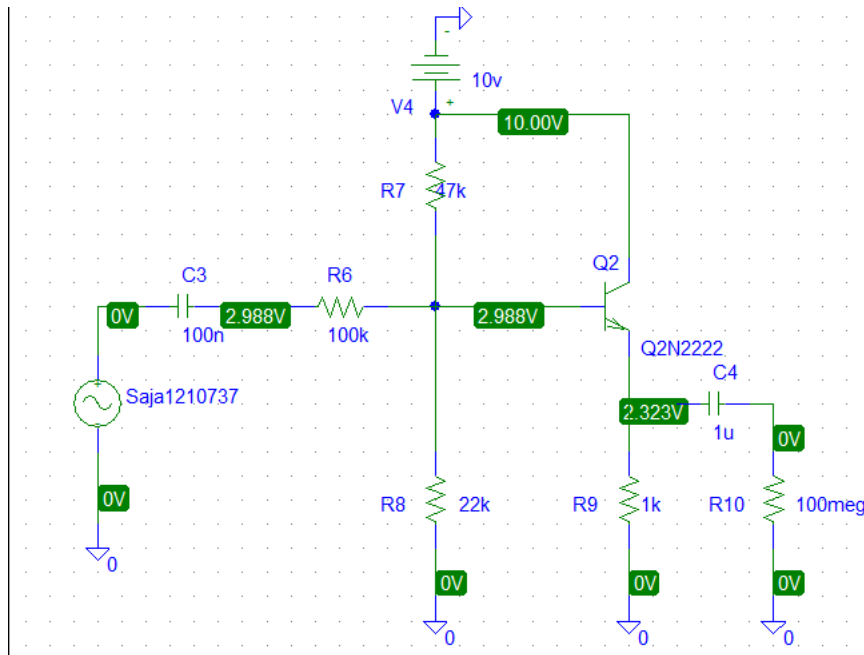


Figure 16:CC circuit voltage

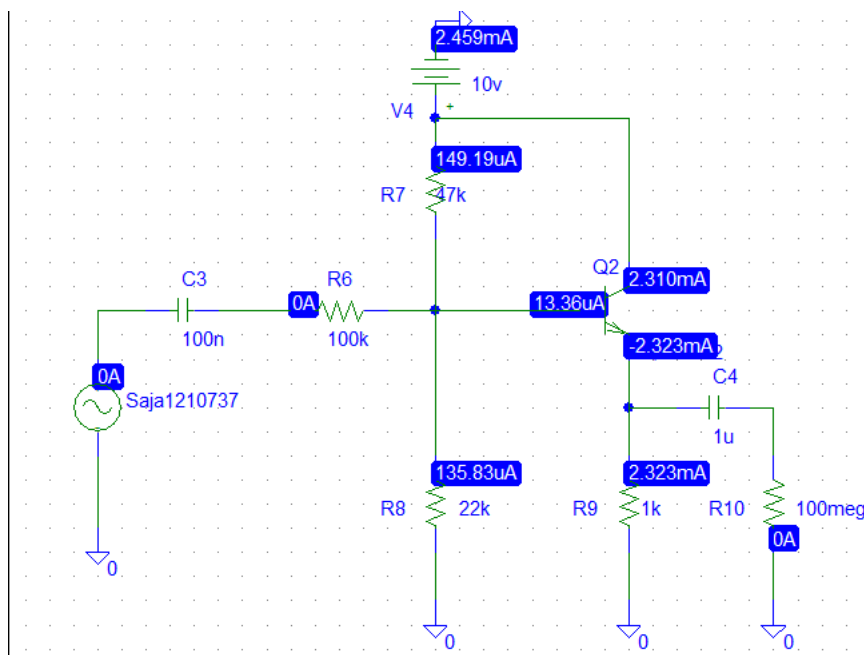


Figure 17:CC circuit Current

$V_B = 2.988V$, $V_C = 10V$, $I_B = 13.36\mu A$, $I_C = 2.310\text{ mA}$.

In order to get the input voltage that gives an output voltage 2volts peaks-peak, the voltage gain must be calculated, so the input voltage will be 1V amplitude in order to see the behavior of the output voltage to calculate the gain. The graph is displayed in the figure below.

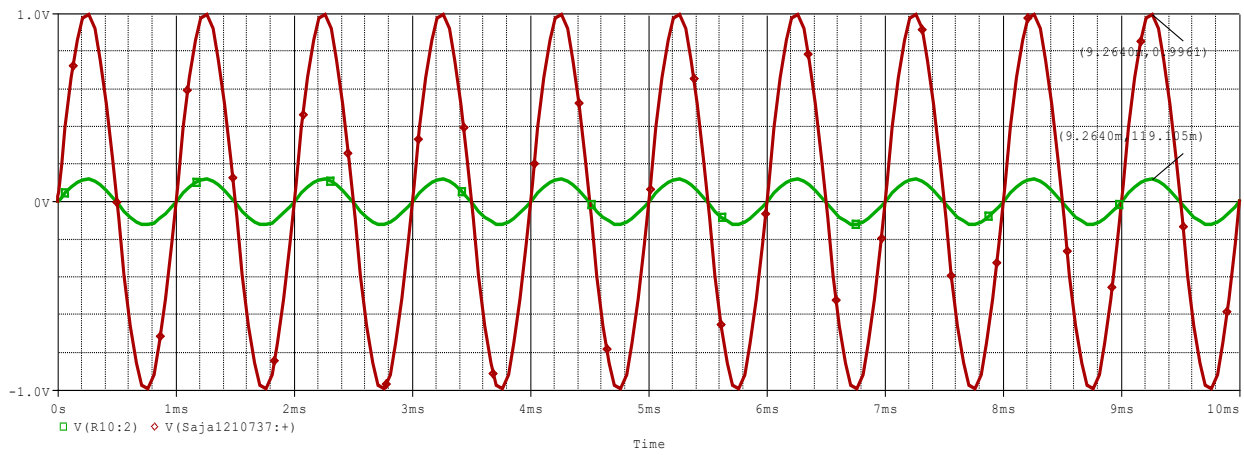


Figure 18:CC Vo and Vi waveforms in order to calculate the gain

$$A_v = V_o/V_i = 119.105\text{mV}/0.9961 = 0.1196$$

So, if $V_o = 2\text{V}$ peak-to-peak (1 volt amplitude) then $V_{in} = 1/0.1196 = 8.3612\text{V}$ amplitude which equals to 16.7224V .

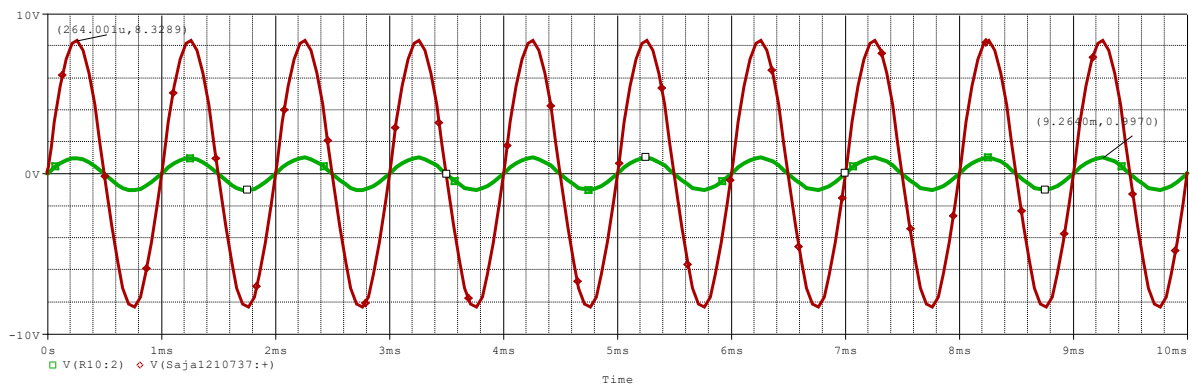


Figure 19:CC Vi and Vo waveforms when $V_o = 2\text{V}$ peak-to-peak

$$V_{out} = 0.9970\text{ V} \approx 1\text{ V} \rightarrow V_{out} = 2\text{ V peak to peak}$$

$$V_{in} = 8.3289 \approx 8.4\text{ V}$$

$$A_V = 0.119$$

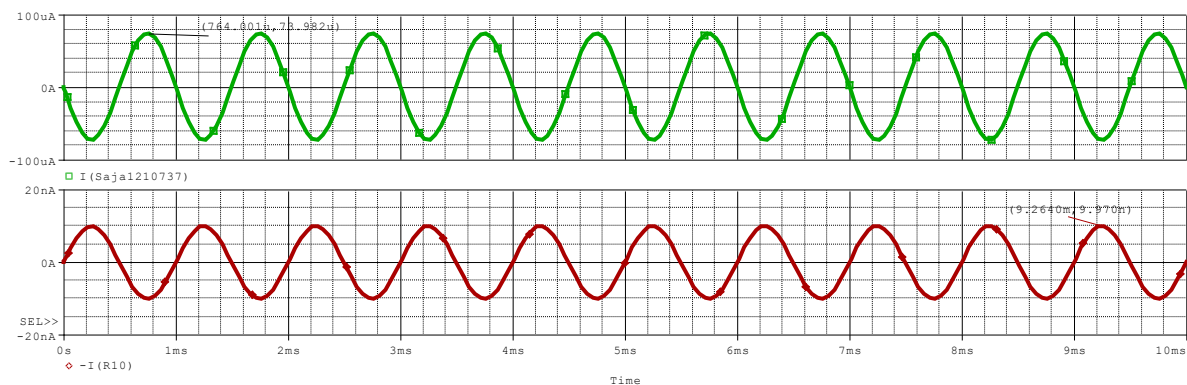


Figure 20:CC Input and output currents

$I_{in}=73.982\mu A$, $I_o=9.972nA$ so the current gain $A_i=I_o/I_{in}=0.1347m$.

$Z_{in}=V_{in}/I_{in}=8.3289/73.982\mu A=112.58k\Omega$.

In order to calculate Z_o , the input voltage source will be replaced by a short circuit, and the source will be added to the output after a capacitor as shown in the figure below.

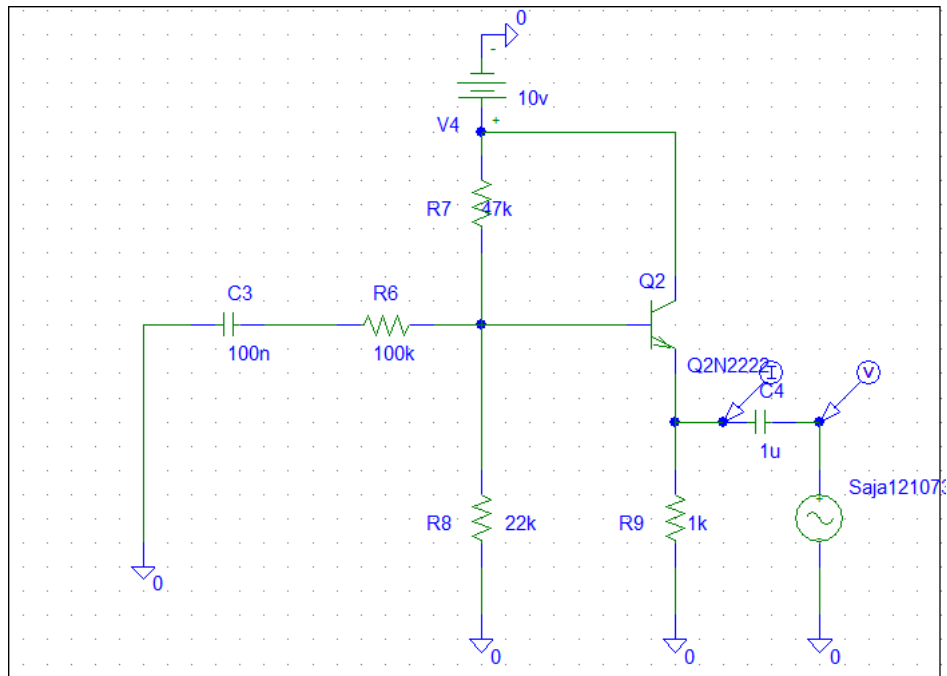


Figure 21:CC Output impedance measuring circuit

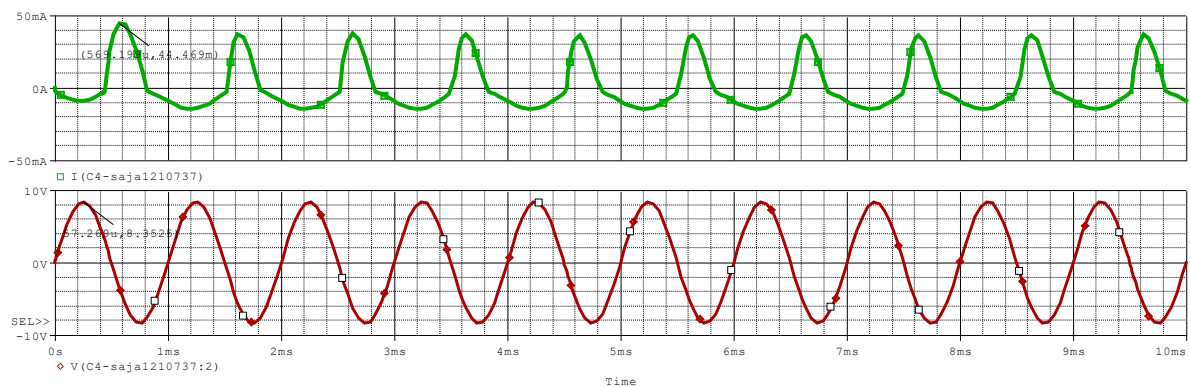


Figure 22:CC output voltage and current for the impedance

$Z_o=V_o/I_o=8.3525/44.469mA=187.8275\Omega$

Table 1: CC measured and calculated value

Quantity	Measured value
V_{in}	8.3289v amplitude
V_{out}	0.9970v amplitude
v100k_RMS	7.3982V amplitude
I_{out}	9.972nA
Calculated Value	
A_v=V_{out}/v_{in}	0.1196 v/v
I_{in} = v100k_RMS /100k	73.982uA
A_i=I_{out}/I_{in}	0.1347m
Z_{in}=V_{in}/I_{in}	112.58kΩ.
Z_{out}=V_t/I_t	187.8275Ω